


Design of a High-performance amplifier with a bandwidth of 500 MHz

By: Over Amaya, Santiago Recalde, Ezequiel
Giorgis, Juan Morán, Leandro Passeti

Outline

- Design Flow
- Specifications and requirements
- Topology of HPA
- Circuit Implementation
- Measurements Open Loop HPA
- Measurements Close Loop HPA


Design flow

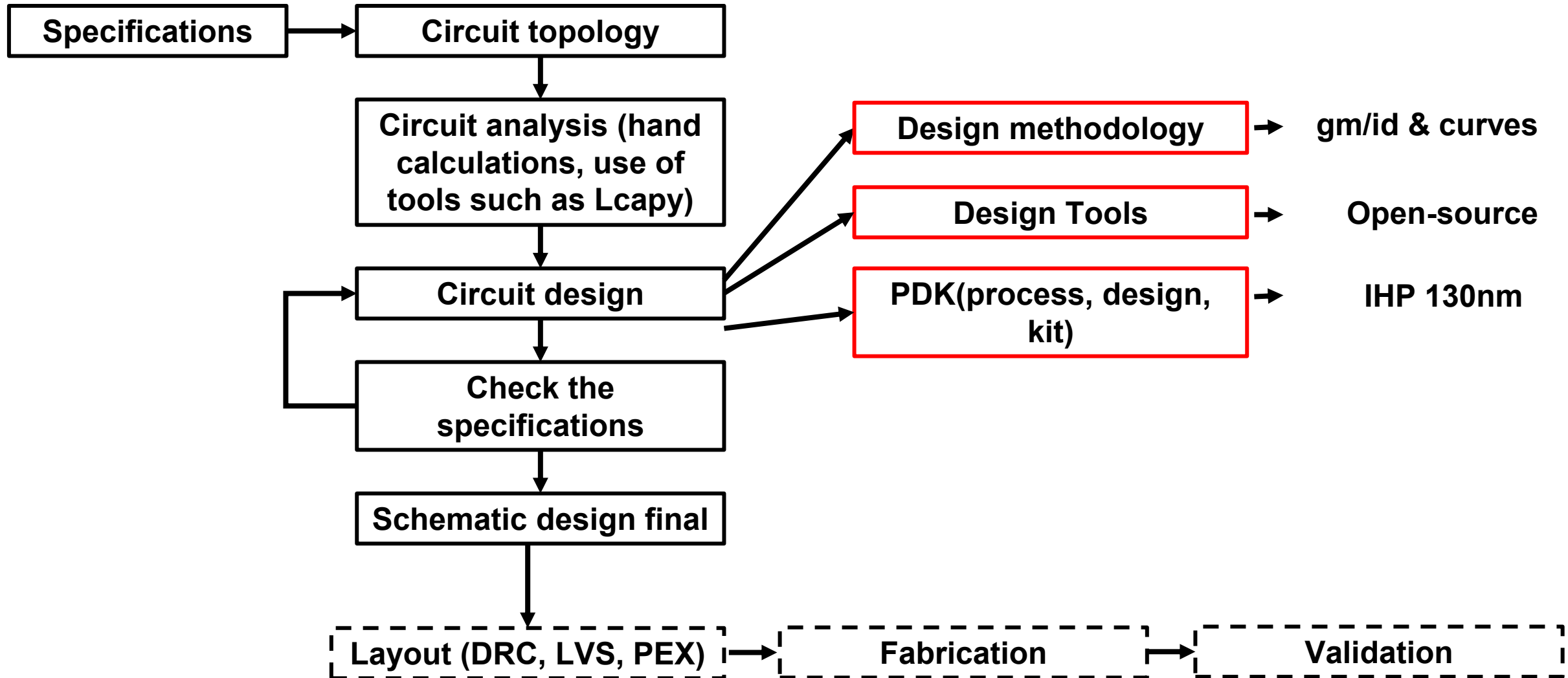

Specifications and requirements

HPA Specifications	
Boundary Conditions	Requirement
Techn.	CMOS
Node	130 nm
Supply Voltage	$1.8 \pm 10\% \text{ V}$
Temperature	$[0, 65, 125] \text{ }^{\circ}\text{C}$
CL	0.5 pF
Bias current	$100 \pm 5\% \text{ uA}$
Output Type	Fully Differential
Specifications	Value
Close loop bandwidth (f_{c-3dB})	$\geq 500 \text{ MHz}$
Close loop gain (A_{vCL})	$7 \pm 0.1 \text{ dB}$
Output Swing	500 mVpp
ENOB @ 100 MHz	$\geq 9 \text{ bits}$
ENOB @ 400 MHz	$\geq 7.5 \text{ bits}$


HPA feedback loop configuration

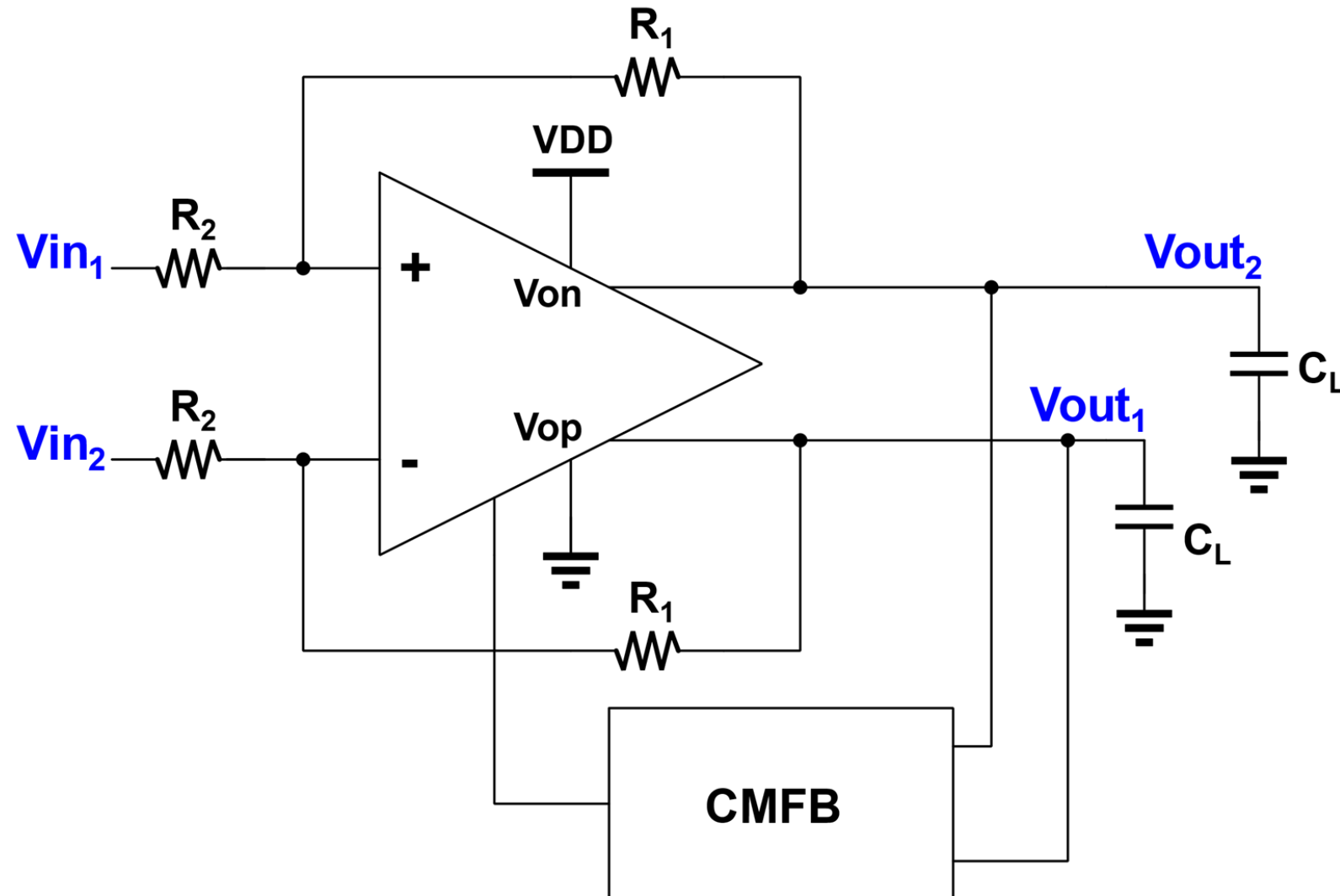


$$A_{vCL} = \frac{R_1}{R_2}$$

$$C_L = 0.5 \text{ pF}$$


Topology of HPA

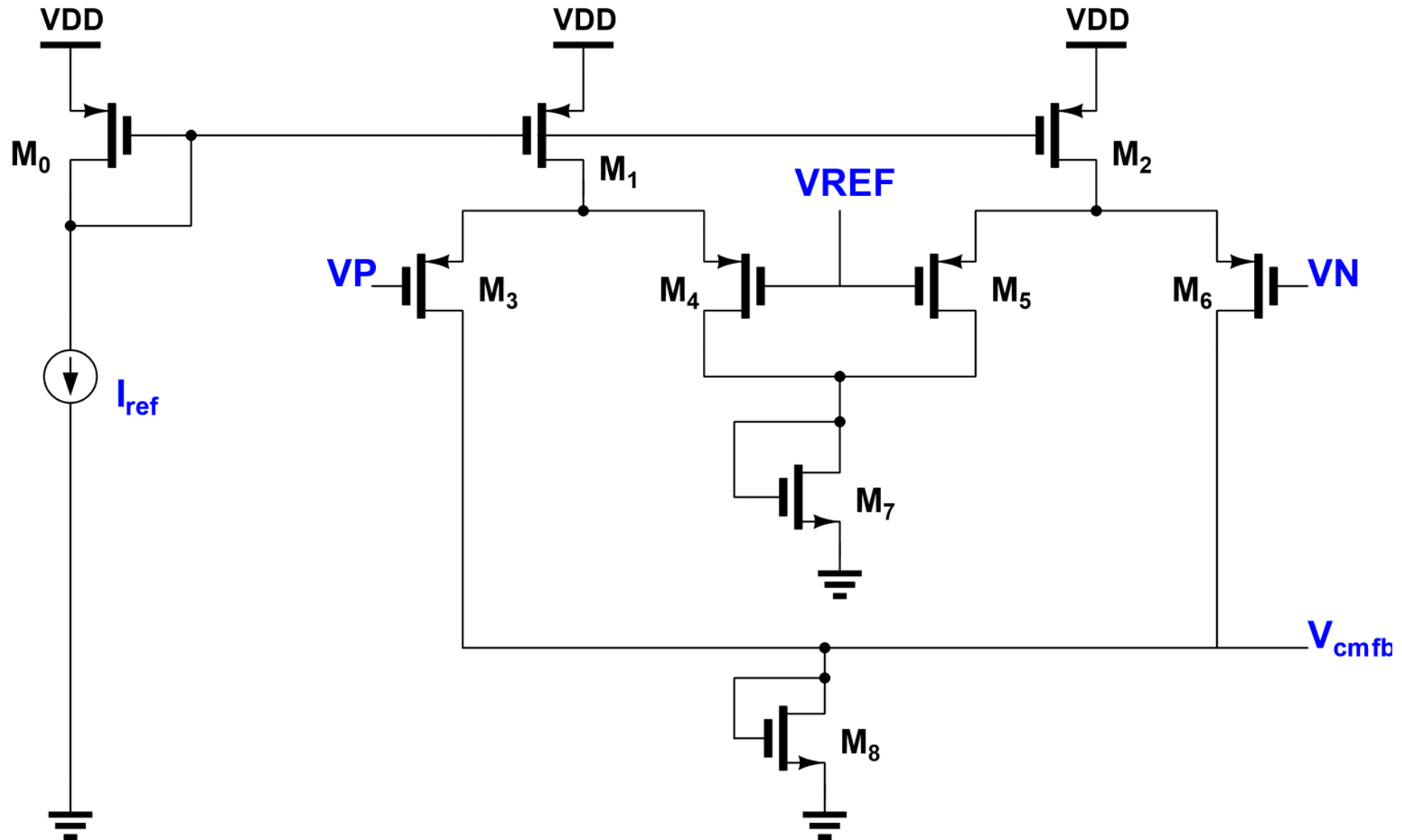

Circuit Implementation

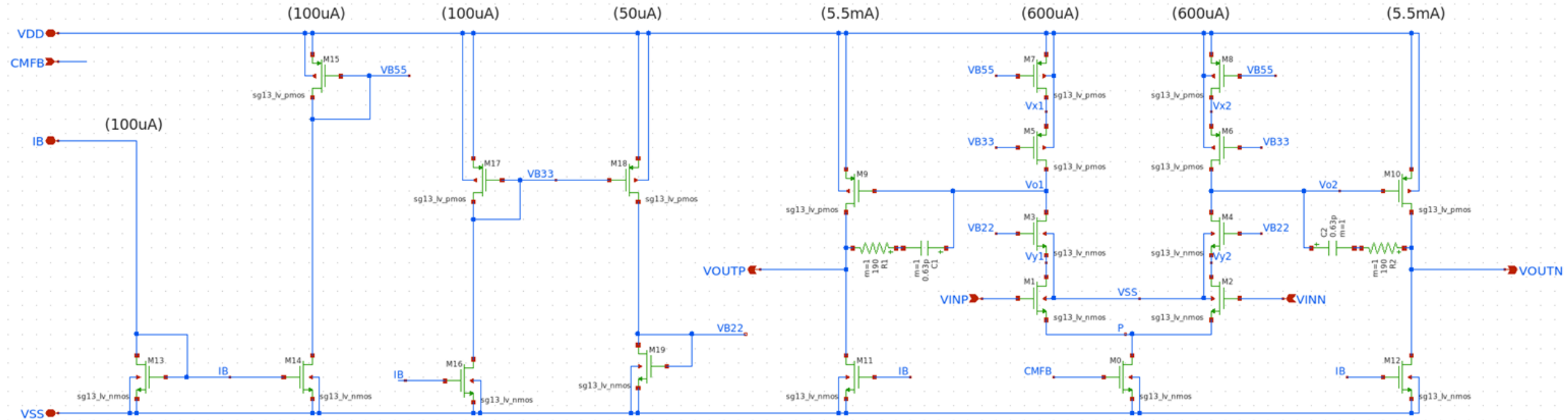

Circuit Implementation

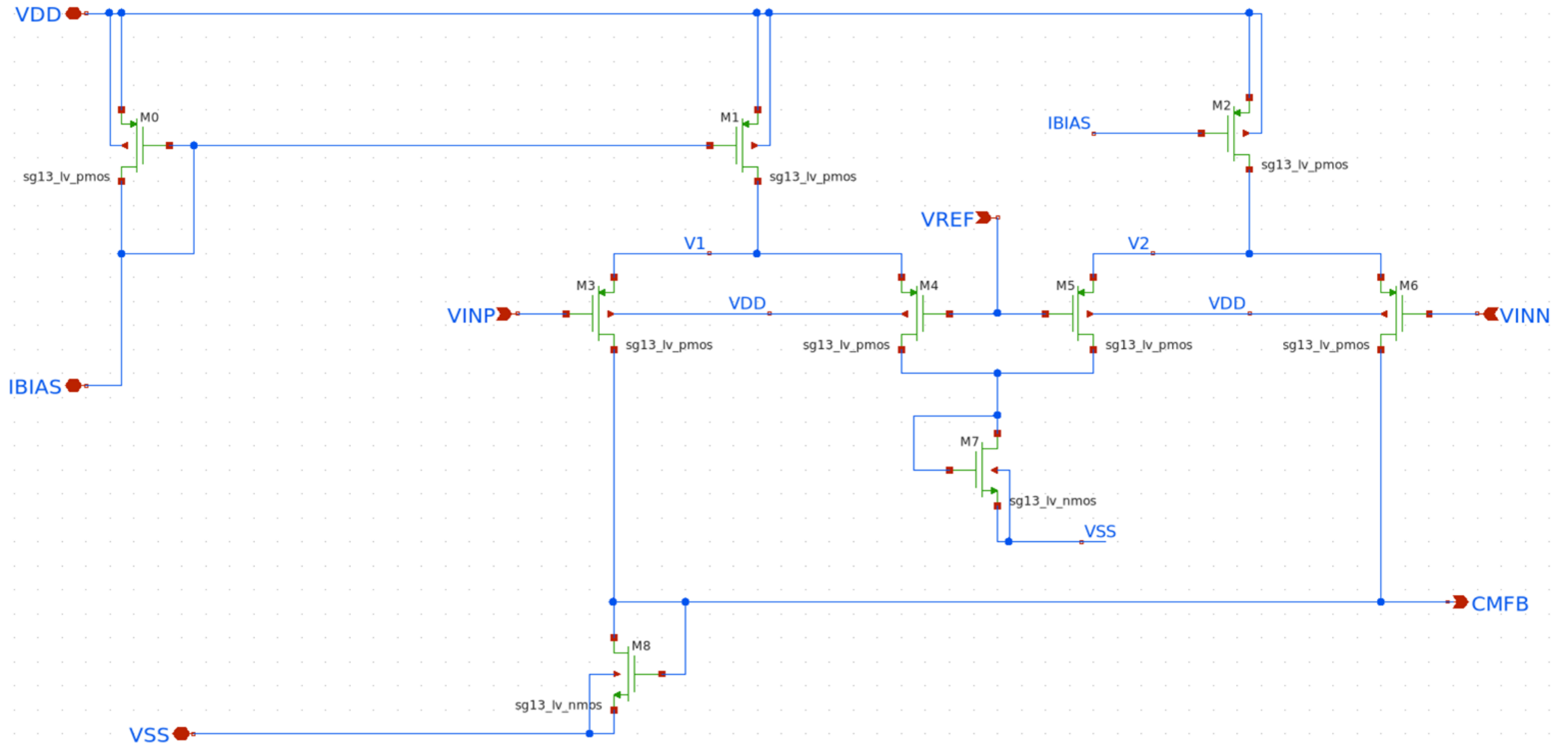


Corners

- PVT(Process, Voltage, Temperature) variations:



Corner	Temperature [°C]	VDD [V]	Iref [uA]
SS: Slow	125	1.62	95
TT: Typical	65	1.8	100
FF: Fast	0	1.98	105

Open loop HPA

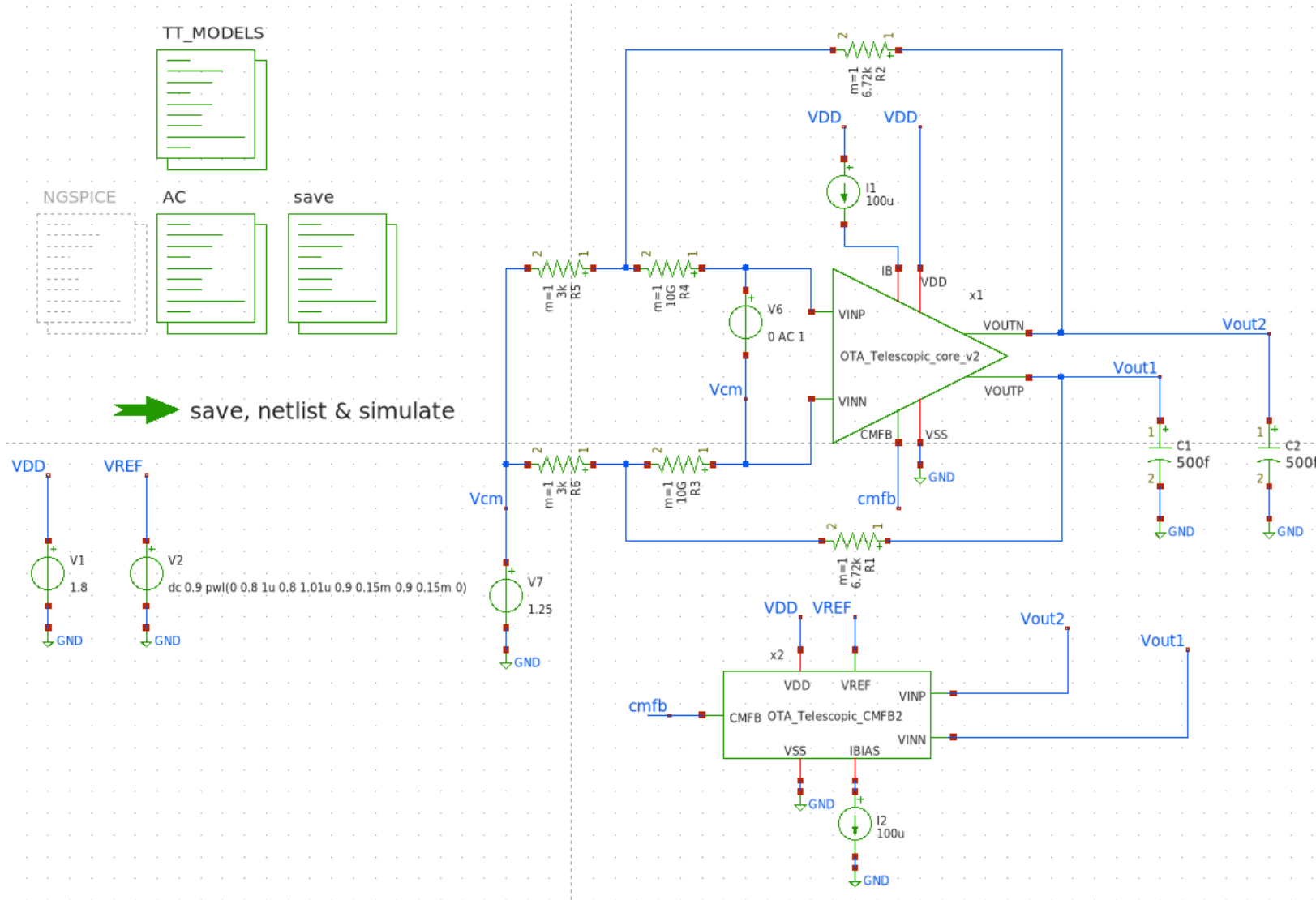


Measurements Open Loop HPA

Spec	Target	Slow	Typical	Fast
Open loop gain (A_{VCL})	≥ 44.35 dB	To do	55.5 dB	To do
Phase Margin	$\geq 60^\circ$	To do	56.2°	To do
Unity Gain Bandwidth (UGB)	≥ 795 MHz	To do	1240 MHz	To do

 
 


Close Loop HPA

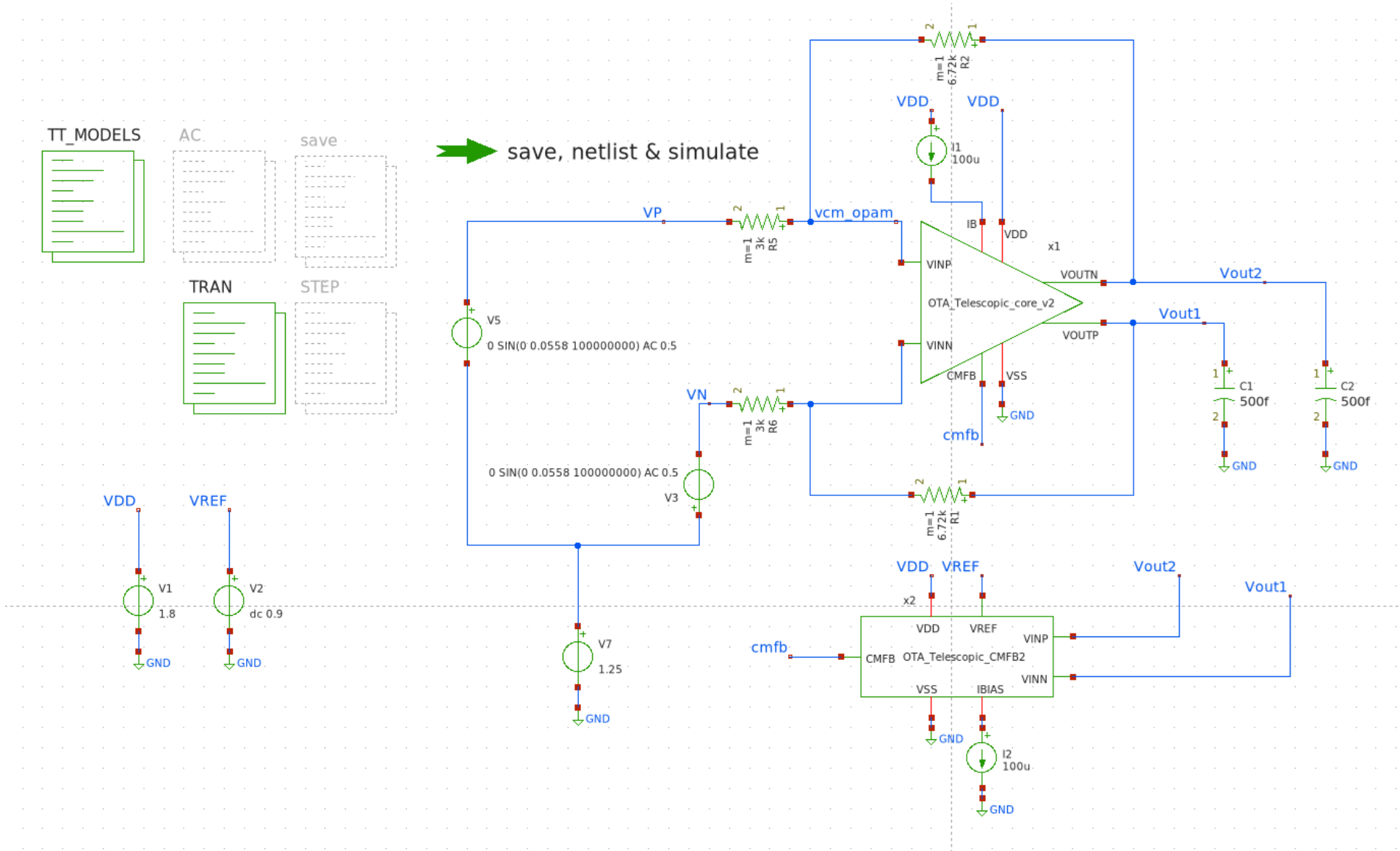



Measurements Close Loop HPA

Spec	Target	Slow	Typical	Fast
Close loop bandwidth (f_{c-3dB})	≥ 500 MHz	To do	796 MHz	To do
Close loop gain (A_{VCL})	7 ± 0.1 dB	To do	6.98 dB	To do

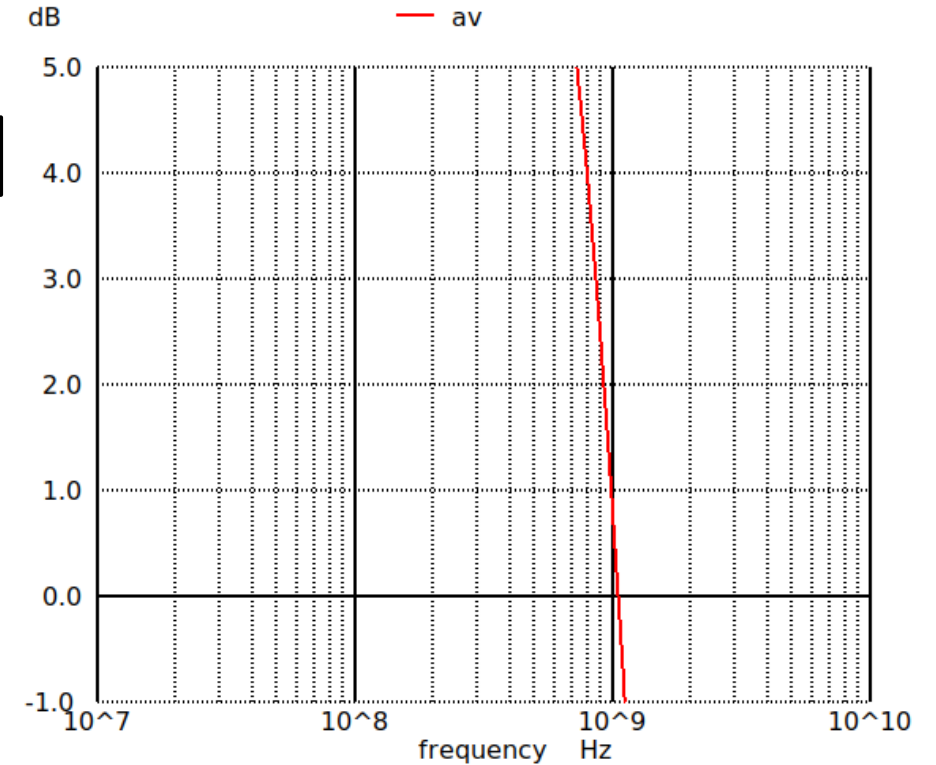 



Measurements Close Loop HPA

Spec	Target	Slow	Typical	Fast
SNDR @ 100 MHz	≥ 55.94 dB	To do	60.11 dB	To do
ENOB @ 100 MHz	≥ 9 bits	To do	9.69 bits	To do

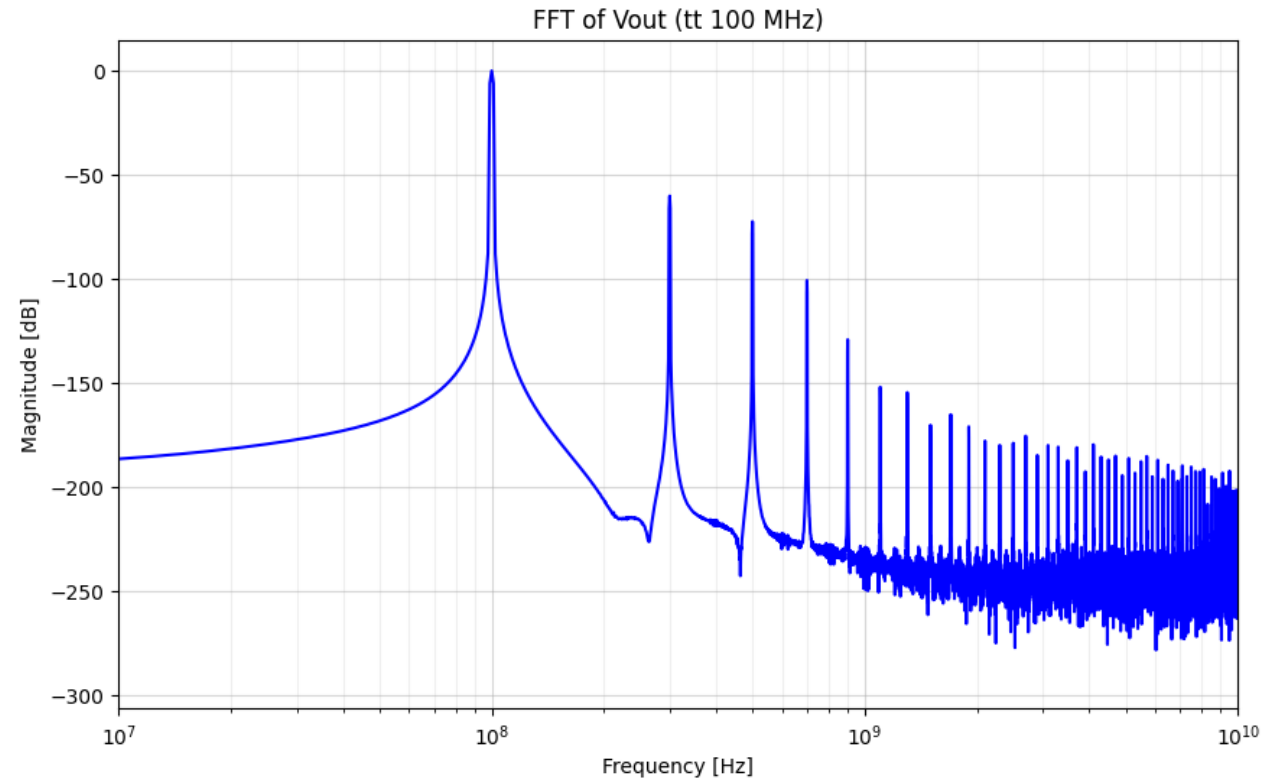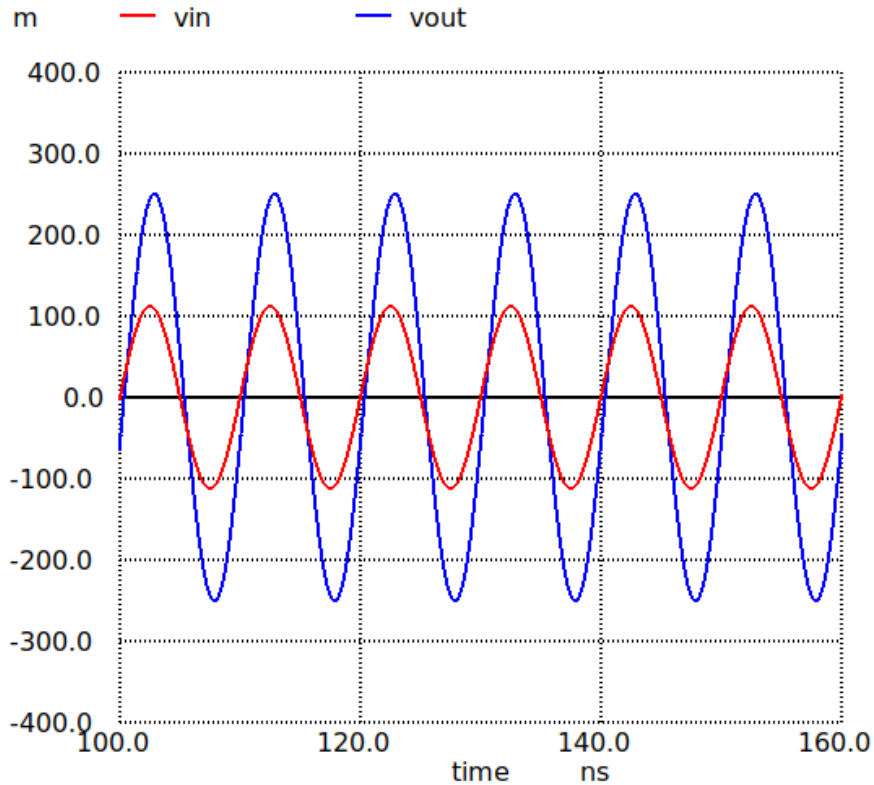

Measurements Close Loop HPA

Spec	Target	Slow	Typical	Fast
SNDR @ 400 MHz	≥ 46.91 dB	To do	53.09 dB	To do
ENOB @ 400 MHz	≥ 7.5 bits	To do	8.53 bits	To do

  

References

- [1] F. Tolosa, E. Dri, Á. F. Bocco and B. T. Reyes, "High Performance Amplifier in 130nm CMOS Technology using an Open Source Design Flow for 10Gbase-T Ethernet Transceivers," 2023 Argentine Conference on Electronics (CAE), Cordoba, Argentina, 2023, pp. 75-80, doi: 10.1109/CAE56623.2023.10087008.
- [2] B. Razavi, Design Of Analog Cmos Integrated Circuit , 2Nd Edition, Mc Graw Hill India, 2017
- [3] P. E. Allen and D. R. Holberg, CMOS Analog Circuit Design, 3rd ed. New York, NY: Oxford University Press, 2011.

Thank you!!!

**overjamaya@gmail.com,
srecaldegm@gmail.com,
ezegiorgis@hotmail.com,
juancruz1887@gmail.com,
leandropassetti@gmail.com**